

General Description

It is a common practice to capacitively couple Ethernet transceivers (PHYs) together without the use of a transformer to reduce both the BOM cost and PCB area. This application note describes methods for capacitive coupling of Micrel's 10/100 Ethernet devices.

Micrel Devices for Capacitive Coupling

KS8695X	CENTAUR – Integrated Multi-port Gateway Solution
KS8695P/PX	CENTAUR – Integrated Multi-port PCI Gateway Solution
KS8721B/BT	Single Port 10/100 PHY with Auto MDI/MDI-X Crossover
KS8721BL/SL	3.3V Single Power Supply 10/100 PHY with Auto MDI/MDI-X Crossover
KS8993	3-Port 10/100 Unmanaged Switch
KS8993F	3-Port 10/100 Managed/Unmanaged Switch/Media Converter with TS-1000 OAM
KS8993M	3-Port 10/100 Managed/Unmanaged Switch
KS8995M/X	5-Port 10/100 Managed/Unmanaged Switch
KS8995MA/XA	5-Port 10/100 Managed/Unmanaged Switch
KS8997	8-Port 10/100 Unmanaged Switch
KS8999	9-Port 10/100 Unmanaged Switch

Methods for Capacitive Coupling

The method for capacitive coupling depends upon whether or not the receiver circuit provides an internal DC bias offset.

Transmit Termination

Figures 1 and 2 show the capacitive coupling for transmit-side termination. In this method, the 50Ω pull-up resistors R1 and R2 are pulled up to analog V_{DD}. All Micrel devices listed in this application note require this output termination, except for the KS8993 device.

For the KS8993, R1 and R2 are tied together, but not to V_{DD}. The TXPx and TXMx differential signals are each terminated with 50Ω pull-ups to the port's VREFx pin.

Receive Termination for Devices with Internal DC Bias

Figure 1 shows the circuit diagram for capacitive coupling to a receiver with internal DC biasing. The 50Ω pull-up resistors R3 and R4 are capacitively coupled via C3 to analog V_{DD}, providing the correct receiver input termination. This method is applicable to the KS8993, which provides internal DC biasing.

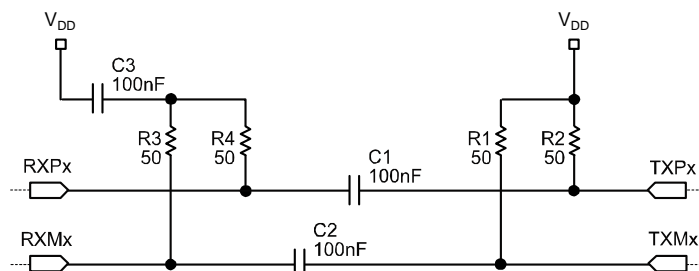


Figure 1. Capacitive Coupling Circuit Diagram for Receivers with Internal DC Bias

Receive Termination for Devices without Internal DC Bias

Figure 2 shows the circuit diagram for capacitive coupling to a receiver without internal DC biasing. In this illustration, the 50Ω pull-up resistors R3 and R4 on the receiver inputs provide the necessary DC offset. These 50Ω resistors also provide the input termination.

This method is applicable to the KS8695X, KS8695P/PX, KS8721B/BT, KS8721BL/SL, KS8993M/F, KS8995M/X, and KS8995MA/XA, none of which provide internal DC biasing.

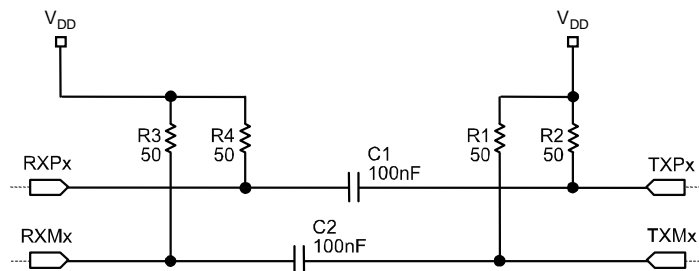


Figure 2. Capacitive Coupling Circuit Diagram for Receivers without Internal DC Bias

Transmit /Receive Termination for KS8997 and KS8999

Figure 2 shows the capacitively coupling between two KS8997 or KS8999 devices. It is necessary to choose pull up resistor values (R1, R2, R3, and R4) that will provide the DC offset for the transmit differential pair Txdc level greater than 1.3V in order to maintain a reasonable and balanced swing. To accomplish this, the following values should be utilized:

$$V_{DD} = 2.1V \text{ (typ)}$$

$$R1, R2, R3, R4 = 33 \text{ ohms}$$

$$Txdc = 1.44V \text{ (} V_{DD} - 20mA \times 33ohms \text{)}$$

$$\text{Swing} = \pm 330mV \text{ (} 20mA \times 33/2 \text{ ohms)}$$

or

VDD = 2.3V(max)

R1, R2, R3, R4 = 40 ohms

Txd_c = 1.5V (VDD-20mA x 40ohms)

Swing = +/- 400mV (20mA x 40/2 ohms)

Using these values will provide a reliable capacitively coupled circuit between two KS8997 or KS8999 devices over a short distance.

Recommended Link Configuration

Configure both link partners as follows:

Force Mode (auto-negotiation disabled)

Auto MDI/MDI-X (disabled)

100BASE-TX

The only exception to this recommendation is the KS8997. The KS8997 does not support force mode and auto-negotiation must be performed. Auto-negotiation has been verified under these circumstances.

The designer can choose either half-duplex or full-duplex mode.

100BASE-TX Applications

For 100BASE-TX, the transmit drivers are current-driven for all the Micrel devices discussed in this application note.

The transmit side drives at 20mA single-ended. If the supply voltage for the 100BASE-TX transmitters and the transmit side pull-up resistors (R1, R2) is 2.5V, the DC offset for the transmit differential pair is 1.5V ($2.5V - (0.02A \times 50\Omega) = 1.5V$).

On the receive side, the receive differential pair has a very high input impedance. If the supply voltage for the 100BASE-TX receivers and receive-side pull-up resistors (R3, R4) is 2.5V, the

DC offset for the receive differential pair will still be approximately 2.5V.

10BASE-T Applications

If 10BASE-T configuration is required, the given methods for capacitive coupling are valid only if the 10BASE-T transmitter circuit design is voltage driven. The KS8695X, KS8695P/PX, KS8993, KS8993M/F, and KS8995MA/XA all have voltage drive 10BASE-T transmitter circuitry.

When using the standard 50Ω termination, current drive 10BASE-T transmitters are unable to provide a full 2.3V output amplitude swing. For example, with a 50mA output drive and two 50Ω pull-up resistors (R1, R2), the voltage drop is 2.5V ($0.05A \times 50\Omega = 2.5V$); thus, the signal is fully attenuated. To increase the output voltage swing at the receiver, it is recommended to implement the following resistor changes:

R1, R2 = 15Ω

R3, R4 = 75Ω

Using this method provides a voltage swing greater than the minimum 400mV receiver squelch threshold. The consequence of altering the pull-up resistor values to provide a minimum output voltage swing is a slight mismatch in the termination impedance. Signal traces should be kept to a minimum length to avoid poor signal integrity. The KS8721B/BT, KS8721BL/SL, KS8995M/X, KS8997, and KS8999 all have current drive 10BASE-T transmitter circuitry.

For additional information, contact your local Micrel Field Application Engineer or salesperson.

MICREL, INC. 2180 FORTUNE DRIVE SAN JOSE, CA 95131 USA
 TEL +1 (408) 944-0800 FAX +1 (408) 474-1000 WEB <http://www.micrel.com>

The information furnished by Micrel in this data sheet is believed to be accurate and reliable. However, no responsibility is assumed by Micrel for its use. Micrel reserves the right to change circuitry and specifications at any time without notification to the customer.

Micrel Products are not designed or authorized for use as components in life support appliances, devices or systems where malfunction of a product can reasonably be expected to result in personal injury. Life support devices or systems are devices or systems that (a) are intended for surgical implant into the body or (b) support or sustain life, and whose failure to perform can be reasonably expected to result in a significant injury to the user. A Purchaser's use or sale of Micrel Products for use in life support appliances, devices or systems is a Purchaser's own risk and Purchaser agrees to fully indemnify Micrel for any damages resulting from such use or sale.

© 2004 Micrel, Incorporated.